

DSP48A1

by Ahmed Khalaf Mohamed Ali

Under the guidance of **Eng. Kareem Waseem**

OVERVIEW

Description

This project centers on the design and implementation of a DSP48A1 slice within a Spartan-6 FPGA, aimed at supporting computation-heavy applications. The DSP48A1 slice is a specialized hardware unit designed to handle complex digital signal processing (DSP) functions such as multiplication, addition, and accumulation. It is particularly well-suited for high-performance tasks requiring efficient arithmetic operations.

Key Features


Optimized DSP48A1 Slice Implementation: The project delivers an optimized implementation of the DSP48A1 slice within the Spartan-6 FPGA. By incorporating advanced pipelining techniques, the design significantly enhances processing speed and efficiency for complex arithmetic computations, making it ideal for intensive digital signal processing tasks.

Advanced Vivado Workflow: Leveraging the Vivado design suite, the project follows a rigorous development workflow. This includes detailed elaboration, synthesis, and implementation phases, which ensure that the design meets high standards of reliability and performance, while also minimizing errors through exhaustive simulation and analysis.

Comprehensive Testbench Strategy: The project employs a robust testbench methodology, utilizing sophisticated test patterns to thoroughly verify the functionality of the DSP48A1 slice. This includes testing for accuracy in arithmetic operations, waveform integrity, and meeting timing constraints across various operational scenarios.

Highly Adaptive Configuration Options: The DSP48A1 slice design is engineered for flexibility, featuring a wide range of configurable parameters. Users can adjust pipeline stages and control registers, including AOREG, A1REG, BOREG, and B1REG, to tailor the design to meet specific computational needs. This adaptability makes the design versatile across different application domains, from basic arithmetic to complex DSP operations.

DSP BLOCK DIGRAM

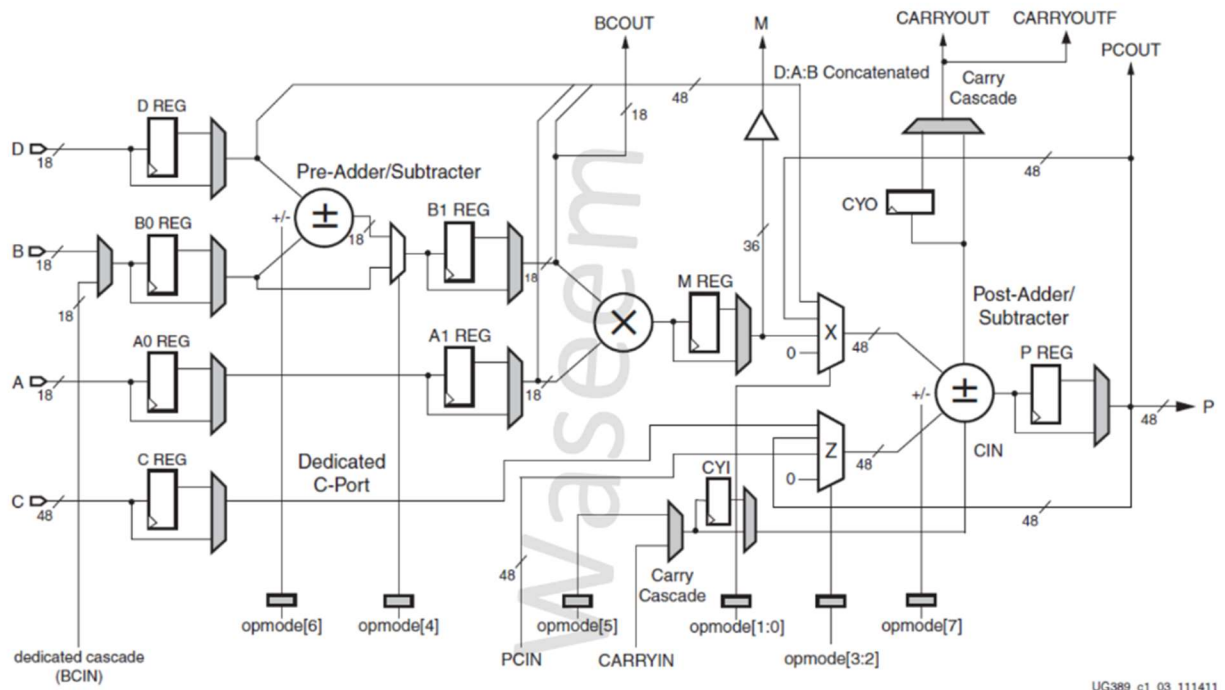

DSP48A1 BLOCK

DSP SLICE

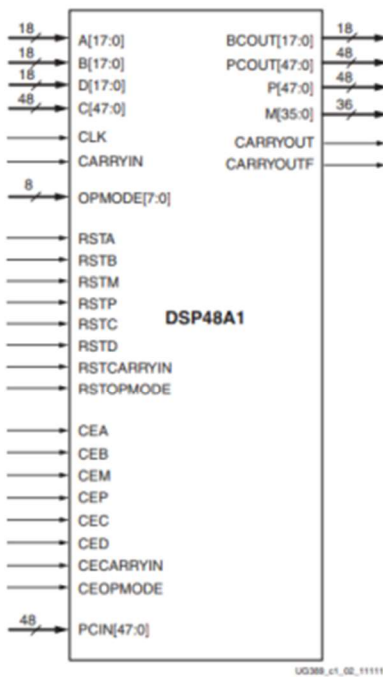


Figure 1-2: DSP48A1 Slice Primitive



SPARTAN. 

DSP48A1:

I make this project with structural modeling Make instance to each block. i will insert all instance codes in end of report

```
21 module DSP_Spartn_six(CLK,OPMODE,A,B,BCIN,PCIN,C,D,CARRYIN,RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE,CEA, CEB, CEM, CEP, CEC,  
22 CED, CECARRYIN, CEOPMODE,BCOUT,PCOUT,P,M,CARRYOUT,CARRYOUTF);  
23 parameter A0REG = 0;  
24 parameter A1REG = 1;  
25 parameter B0REG = 0;  
26 parameter B1REG = 1;  
27 parameter CREG = 1;  
28 parameter DREG = 1;  
29 parameter MREG = 1;  
30 parameter PREG = 1;  
31 parameter CARRYINREG = 1;  
32 parameter CARRYOUTREG = 1;  
33 parameter OPMODEREG = 1;  
34 parameter CARRYINSEL = "OPMODE5";  
35 parameter B_INPUT = "DIRECT";  
36 parameter RSTTYPE = "SYNC";  
37 input CLK;  
38 input [7:0] OPMODE;  
39 input [17:0] A;  
40 input [17:0] B;  
41 input [17:0] BCIN;  
42 input [47:0] PCIN;  
43 input [47:0] C;  
44 input [17:0] D;  
45 input CARRYIN;  
46 input RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE;  
47 input CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;  
48 output [17:0] BCOUT;  
49 output [47:0] PCOUT;  
50 output [47:0] P;  
51 output [35:0] M;  
52 output CARRYOUT;  
53 output CARRYOUTF;
```

```
wire [17:0] Q_A0REG,Q_A1REG;  
wire [17:0] Q_DREG;  
wire [47:0] Q_CREG;  
wire [17:0] Q_B0REG,Q_B1REG;  
wire [7:0] Q_OPMODEREG;  
wire [17:0] pre_add_sub;  
wire [17:0] pre_add_sub_mux;  
wire [35:0] MUL_REG;  
wire [35:0] M_REG;  
wire [47:0] MUX_REGX;  
wire [47:0] MUX_REGZ;  
wire mux_carryin;  
wire MUX_CARRYIN_REG;  
wire [47:0]P_sum;  
wire P_carry;  
wire [47:0]P_sum_reg;  
wire P_carry_reg;
```

```

70 MUX_DFF #(.DFF_SELECT(A0REG),.RSTTYPE(RSTTYPE),.DFF_SIZE(18)) A0REG_DESIGN (.clk(CLK),.rst(RSTA),.enable(CEA),.PIN_IN(A),.PIN_OUT(Q_A0REG));
71 MUX_DFF #(.DFF_SELECT(DREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(18)) DREG_DESIGN (.clk(CLK),.rst(RSTD),.enable(CED),.PIN_IN(D),.PIN_OUT(Q_DREG));
72 MUX_DFF #(.DFF_SELECT(CREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(48)) CREG_DESIGN (.clk(CLK),.rst(RSTC),.enable(CEC),.PIN_IN(C),.PIN_OUT(Q_CREG));
73 MUX_DFF_B #(.DFF_SELECT(B0REG),.RSTTYPE(RSTTYPE),.DFF_SIZE(18),.B_INPUT(B_INPUT)) B0REG_DESIGN (.clk(CLK),.rst(RSTB),.enable(CEB),.PIN_IN(B),.
CASCAD(B0REG),.PIN_OUT(Q_B0REG));
74 MUX_DFF #(.DFF_SELECT(OPMODEREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(8)) OPCODEREG_DESIGN (.clk(CLK),.rst(RSTOPMODE),.enable(CEOPMODE),.PIN_IN
(OPMODE),.PIN_OUT(Q_OPMODEREG));
75 N_BIT_ADDER #(.N(18)) ADDER (.D(Q_DREG),.B(Q_B0REG),.SEL(Q_OPMODEREG[6]),.C(pre_add_sub));
76 mux2x1 #(.N(18)) mux2x1_design(.D0(Q_B0REG),.D1(pre_add_sub),.SEL(Q_OPMODEREG[4]),.Y(pre_add_sub_mux));
77 MUX_DFF #(.DFF_SELECT(A1REG),.RSTTYPE(RSTTYPE),.DFF_SIZE(18)) A1REG_DESIGN (.clk(CLK),.rst(RSTA),.enable(CEA),.PIN_IN(Q_A0REG),.PIN_OUT
(Q_A1REG));
78 MUX_DFF #(.DFF_SELECT(B1REG),.RSTTYPE(RSTTYPE),.DFF_SIZE(18)) B1REG_DESIGN (.clk(CLK),.rst(RSTB),.enable(CEB),.PIN_IN(pre_add_sub_mux),.
PIN_OUT(Q_B1REG));
79 N_BIT_Multiplier #(.N(18)) N_BIT_Multiplier_design (.D(Q_B1REG),.B(Q_A1REG),.Out(MUL_REG));
80 MUX_DFF #(.DFF_SELECT(MREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(36)) MREG_DESIGN (.clk(CLK),.rst(RSTM),.enable(CEM),.PIN_IN(MUL_REG),.PIN_OUT(M_REG));
81 N_BIT_MUX4X1 #(.N(48)) N_BIT_MUX4X1_design(.D0(48'b0),.D1({12'b0,M_REG}),.D2(P),.D3({Q_DREG[11:0],Q_A1REG,Q_B1REG}),.S0(Q_OPMODEREG[0]),.S1
(Q_OPMODEREG[1]),.Y(MUX_REGX));
82 N_BIT_MUX4X1 #(.N(48)) N_BIT_MUX4X1_design2(.D0(48'b0),.D1(PCIN),.D2(P),.D3(Q_CREG),.S0(Q_OPMODEREG[2]),.S1(Q_OPMODEREG[3]),.Y(MUX_REGZ));
83 MUX_CARRYIN #(.DFF_SIZE(1),.CARRY_INPUT(CARRYINSEL)) MUX_CARRYIN_DESIGN (.CASCAD(CARRYIN),.PIN_IN(Q_OPMODEREG[5]),.PIN_OUT(mux_carryin));
84 MUX_DFF #(.DFF_SELECT(CARRYINREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(1)) CARRYIN_DESIGN (.clk(CLK),.rst(RSTCARRYIN),.enable(CECARRYIN),.PIN_IN
(mux_carryin),.PIN_OUT(MUX_CARRYIN_REG));
85 Full_adder_con #(.N(48)) ADDER2 (.A(MUX_REGZ),.B(MUX_REGX),.SEL(Q_OPMODEREG[7]),.CIN(MUX_CARRYIN_REG),.carry(P_carry),.sum(P_sum));
86 MUX_DFF #(.DFF_SELECT(PREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(48)) PREG_DESIGN (.clk(CLK),.rst(RSTP),.enable(CEP),.PIN_IN(P_sum),.PIN_OUT
(P_sum_reg));
87 MUX_DFF #(.DFF_SELECT(CARRYOUTREG),.RSTTYPE(RSTTYPE),.DFF_SIZE(1)) CARRYOUTREG_DESIGN (.clk(CLK),.rst(RSTCARRYIN),.enable(CECARRYIN),.PIN_IN
(P_carry),.PIN_OUT(P_carry_reg));
88 assign BCOUT=Q_B1REG;
89 assign PCOUT=P_sum_reg;
90 assign P=P_sum_reg;
91 assign M=M_REG;
92 assign CARRYOUT=P_carry_reg;
93 assign CARRYOUTF=CARRYOUT;
94 endmodule
95

```

```

timescale 1ns / 1ps
module DSP_spartn_six_tb();
    reg CLK;
    reg [7:0] OPMODE;
    reg [17:0] A;
    reg [17:0] B;
    reg [17:0] BCIN;
    reg [47:0] PCIN;
    reg [17:0] C;
    reg [17:0] D;
    reg CARRYIN;
    reg RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE;
    reg CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
    wire [17:0] BCOUT;
    wire [47:0] PCOUT;
    wire [47:0] P;
    wire [35:0] M;
    wire CARRYOUT;
    wire CARRYOUTF;

```

```
20 // Instantiate the DSP48A1 module
```

```
21 DSP_Spartn_six DSP_instance (
```

```
22     .CLK(CLK),
```

```
23     .OPMODE(OPMODE),
```

```
24     .A(A),
```

```
25     .B(B),
```

```
26     .BCIN(BCIN),
```

```
27     .PCIN(PCIN),
```

```
28     .C(C),
```

```
29     .D(D),
```

```
30     .CARRYIN(CARRYIN),
```

```
31     .RSTA(RSTA),
```

```
32     .RSTB(RSTB),
```

```
33     .RSTM(RSTM),
```

```
34     .RSTP(RSTP),
```

```
35     .RSTC(RSTC),
```

```
36     .RSTD(RSTD),
```

```
37     .RSTCARRYIN(RSTCARRYIN),
```

```
38     .RSTOPMODE(RSTOPMODE),
```

```
39     .CEA(CEA),
```

```
40     .CEB(CEB),
```

```
41     .CEM(CEM),
```

```
42     .CEP(CEP),
```

```
43     .CEC(CEC),
```

```
44     .CED(CED),
```

```
45     .CECARRYIN(CECARRYIN),
```

```
46     .CEOPMODE(CEOPMODE),
```

```
47     .BCOUT(BCOUT),
```

```
48     .PCOUT(PCOUT),
```

```
49     .P(P),
```

```
50     .M(M),
```

```
51     .CARRYOUT(CARRYOUT),
```

```
52     .CARRYOUTF(CARRYOUTF)
```

```
53 );
```

```
54     integer i=0;
55     integer TC=200;
56     // Clock generation
57     initial begin
58         CLK = 0;
59         forever #(TC/2) CLK = ~CLK;
60     end
61     initial begin
62         OPMODE = 8'b00000000;
63         A = 18'b0000000000000000;
64         B = 18'b0000000000000000;
65         BCIN = 18'b0000000000000000;
66         PCIN = 48'b000000000000000000000000000000000000000000000000;
67         C = 48'b000000000000000000000000000000000000000000000000;
68         D = 18'b0000000000000000;
69         CARRYIN = 0;
70         RSTA = 1;
71         RSTB = 1;
72         RSTM = 1;
73         RSTP = 1;
74         RSTC = 1;
75         RSTD = 1;
76         RSTCARRYIN = 1;
77         RSTOPMODE = 1;
78         CEA = 1;
79         CEB = 1;
80         CEM = 1;
81         CEP = 1;
82         CEC = 1;
83         CED = 1;
84         CECARRYIN = 1;
85         CEOPMODE = 1;
86
```


[illegible]

```


116   OPMODE = 8'b00000100;
117   @(negedge CLK)
118   A = 18'b00000000000000101;
119   B = 18'b0000000000000010;
120   OPMODE = 8'b10001000;
121   @(negedge CLK) ;
122   for (i=0; i<20 ; i=i+1) begin
123       OPMODE = $random;
124       A = $urandom_range(1,10);
125       B = $urandom_range(1,10);
126       BCIN = $urandom_range(1,10);
127       PCIN = $random;
128       C = $urandom_range(1,10);
129       D = $urandom_range(1,10);
130       CARRYIN = $random;
131   @(negedge CLK);
132   end
133   @(negedge CLK);
134   $stop;
135   end
136
137   endmodule

```


```

1  vlib work
2  vlog  DSP_Spartn_six.v ADDER_SUB.v  DSP_Spartn_six_tb.v N_BIT_Multiplier.v mux2X1.v N_BIT_MUX4X1.v MUX_CARRYIN.v MUX_DFF.v MUX_DFF_B.v Full_adder_con.v
3  vsim -voptargs=+acc work.DSP_Spartn_six_tb
4  add wave *
5  run -all
6  #quit -sim


```

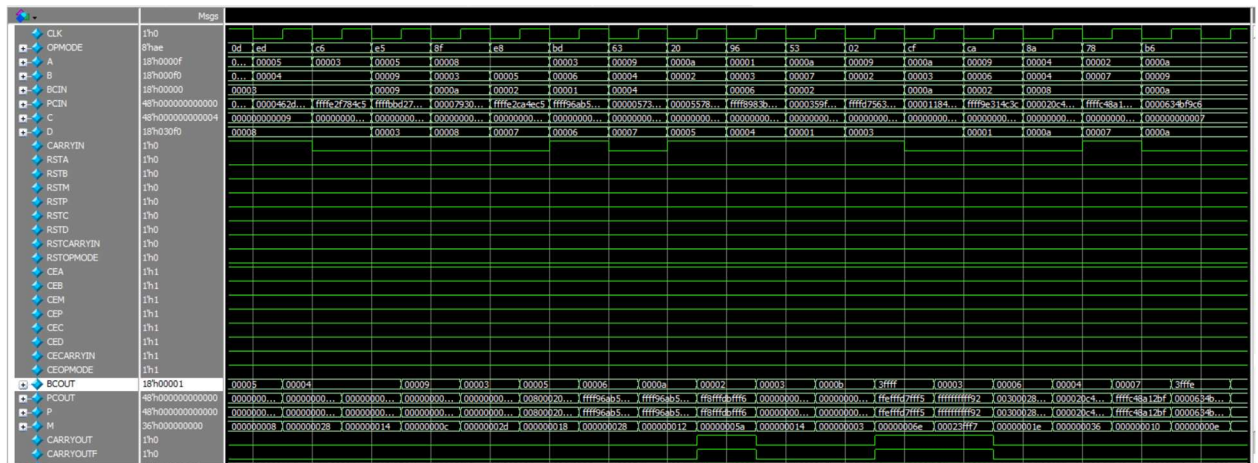

Schematic after elaboration:

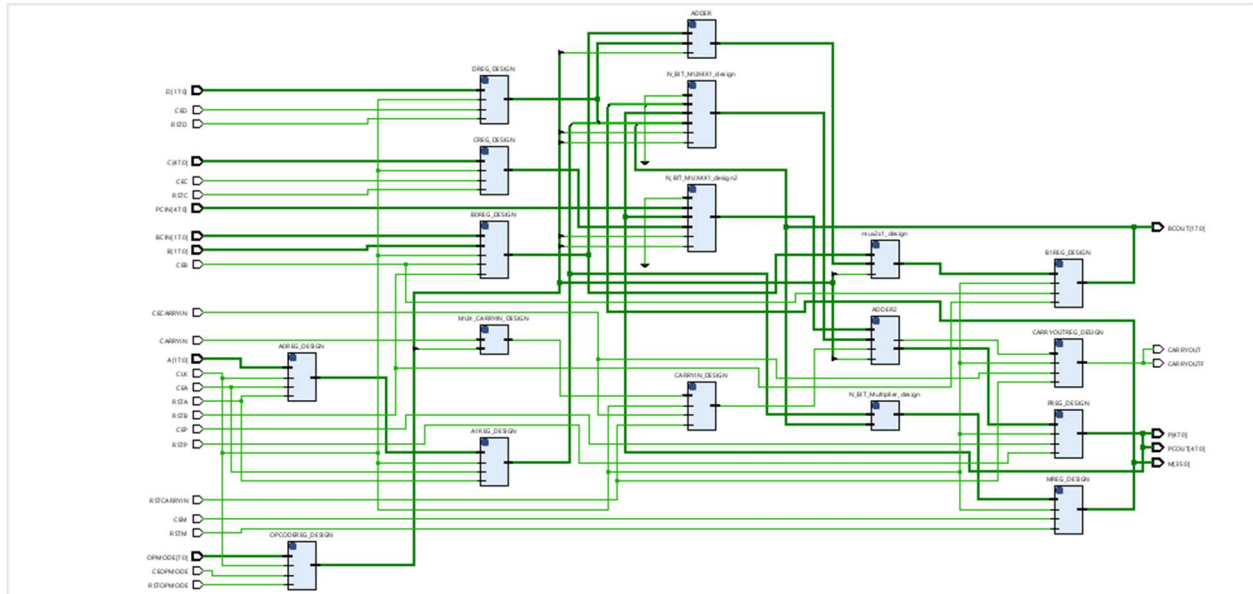

Schematic after synthesis:

 

Report utilization after synthesis:

Utilization						
Hierarchy						
	Name	Slice LUTs (20800)	Slice Registers (41600)	DSPs (90)	Bonded IOB (106)	BUFGCTRL (32)
▼ Hierarchy	▼ DSP_Spartn_six	206	158	1	326	1
▼ Slice Logic	▼ A1REG_DESIGN (MUX_DFF_parameterized0)	0	18	0	0	0
▼ Slice LUTs (1%)	▼ ADDER2 (Full_adder_con)	24	0	0	0	0
▼ LUT as Logic (1%)	▼ B1REG_DESIGN (MUX_DFF_parameterized0_0)	0	18	0	0	0
▼ Slice Registers (1%)	▼ CARRYOUTREG_DESIGN (MUX_DFF_parameterized4)	0	1	0	0	0
▼ Register as Flip Flop (1%)	▼ CREG_DESIGN (MUX_DFF_parameterized1)	0	48	0	0	0
Memory	▼ DREG_DESIGN (MUX_DFF_parameterized0_1)	0	18	0	0	0
▼ DSP	▼ MREG_DESIGN (MUX_DFF_parameterized3)	0	0	1	0	0
▼ DSPs (1%)	▼ mux2x1_design (mux2X1)	19	0	0	0	0
▼ DSP48E1 only	▼ N_BIT_MUX4X1_design (N_BIT_MUX4X1)	1	0	0	0	0
▼ IO and GT Specific	▼ N_BIT_MUX4X1_design2 (N_BIT_MUX4X1_2)	49	0	0	0	0
▼ Bonded IOB (>100%)	▼ OPCODEREG_DESIGN (MUX_DFF_parameterized2)	113	7	0	0	0
▼ IOB Master Pads	▼ PREG_DESIGN (MUX_DFF_parameterized1_3)	0	48	0	0	0
▼ Clocking						
▼ BUFGCTRL (3%)						
Specific Feature						
Primitives						
Black Boxes						
Instantiated Netlists						

Report messages after synthesis:

Tcl Console	Messages	Log	Reports	Design Runs
<div> <input checked="" type="checkbox"/> Info (56) <input type="checkbox"/> Status (25) <button>Show All</button> </div>				
▼ Vivado Commands (3 infos)	Close			
▼ General Messages (3 infos)	<div> <p>[IP_Flow 19-234] Refreshing IP repositories</p> <p>[IP_Flow 19-1704] No user IP repositories specified</p> <p>[IP_Flow 19-2313] Loaded Vivado IP repository 'D:/Vivado/Vivado/2020.2/data/ip'.</p> </div>			
▼ Elaborated Design (1 info)	<div> <p>[Project 1-570] Preparing netlist for logic optimization</p> </div>			
▼ Synthesis (46 infos)	<div> <p>[Common 17-349] Got license for feature 'Synthesis' and/or device 'xc7a35ti'</p> </div>			

instance codes:

```
module N_BIT_MUX4X1(D0,D1,D2,D3,S0,S1,Y);
parameter N=48;
input [N-1:0]D0,D1,D2,D3;
input S0,S1;
output reg [N-1:0] Y;
always @(*) begin
case ({S0,S1})
2'b00 : Y=D0;
2'b01 : Y=D1;
2'b10 : Y=D2;
2'b11 : Y=D3;
endcase
end
endmodule
```

```
module mux2X1(D0,D1,SEL,Y);
parameter N=18;
input [N-1:0]D0,D1;
input SEL;
output reg [N-1:0] Y;
always @(*)
begin
if (SEL)
Y = D1;
else
Y = D0;
end
endmodule
```



```
module MUX_CARRYIN(CASCADE,PIN_IN,PIN_OUT);
parameter DFF_SIZE=1;
parameter CARRY_INPUT = "OPCODE5";
input [DFF_SIZE-1:0]CASCADE;
input [DFF_SIZE-1:0]PIN_IN;
output reg [DFF_SIZE-1 :0]PIN_OUT;
always @(*) begin
if(CARRY_INPUT == "OPCODE5")
PIN_OUT=PIN_IN;
else if(CARRY_INPUT == "CARRYIN")
PIN_OUT=CASCADE;
else
PIN_OUT=0;
end
endmodule
```



```

45 module MUX_DFF(clk,rst,enable,PIN_IN,PIN_OUT);
46 parameter DFF_SELECT=1;
47 parameter RSTTYPE="SYNC";
48 parameter DFF_SIZE=18;
49 input clk,rst,enable;
50 input [DFF_SIZE-1:0]PIN_IN;
51 output reg [DFF_SIZE-1 :0]PIN_OUT;
52 generate
53 case (DFF_SELECT)
54 0: begin
55     always @(*) begin
56         PIN_OUT=PIN_IN;
57     end
58 end
59 1: begin
60 if(RSTTYPE=="SYNC") begin
61     always @(posedge clk) begin
62         if(rst)
63             PIN_OUT<=0;
64         else if (enable)
65             PIN_OUT<=PIN_IN;
66         end
67     end
68 else if (RSTTYPE=="ASYN") begin
69 always @(posedge clk or posedge rst ) begin
70     if(rst)
71         PIN_OUT<=0;
72     else if (enable)
73         PIN_OUT<=PIN_IN;
74     end
75 end
76
77 end
78 endcase
79 endgenerate
80 endmodule

```

```

23 module MUX_DFF_B(clk,rst,enable,CASCADE,PIN_IN,PIN_OUT);
24 parameter DFF_SELECT=1;
25 parameter RSTTYPE="SYNC";
26 parameter DFF_SIZE=18;
27 parameter B_INPUT = "CASCADE";
28 input clk,rst,enable;
29 input [DFF_SIZE-1:0]CASCADE;
30 input [DFF_SIZE-1:0]PIN_IN;
31 output reg [DFF_SIZE-1 :0]PIN_OUT;
32 generate
33 case (DFF_SELECT)
34 0: begin
35     always @(*) begin
36         if ( B_INPUT == "DIRECT") PIN_OUT<=PIN_IN;
37         else if (B_INPUT == "CASCADE") PIN_OUT<=CASCADE;
38     end
39 end
40 1: begin
41 if(RSTTYPE=="SYNC") begin
42     always @(posedge clk) begin
43         if(rst) PIN_OUT<=0;
44         else if (enable) begin
45             if ( B_INPUT == "DIRECT") PIN_OUT<=PIN_IN;
46             else if (B_INPUT == "CASCADE") PIN_OUT<=CASCADE;
47         end end end
48 else if (RSTTYPE=="ASYNC") begin
49     always @(posedge clk or posedge rst ) begin
50         if(rst)
51             PIN_OUT<=0;
52         else if (enable) begin
53             if ( B_INPUT == "DIRECT")
54                 PIN_OUT<=PIN_IN;
55             else if (B_INPUT == "CASCADE")
56                 PIN_OUT<=CASCADE;
57         end end endend
58 endcase endgenerate
59 endmodule

```

```

module Full_adder_con( A,CIN,B,SEL,carry,sum);
parameter N=48;
input [N-1:0] A,B;
input CIN,SEL;
output reg carry;
output reg [N-1:0]sum;
always @(*) begin
if (SEL)
{carry,sum}=A+B+CIN;
else
{carry,sum}=A-(B+CIN);
end
endmodule

```

```
module N_BIT_Multiplier (B,D,Out);  
parameter N=18;  
localparam N_local=2*N;  
input  [N-1:0] B;  
input  [N-1:0] D;  
output [N_local-1:0] Out;  
reg [N_local-1:0]out_reg;  
always @(*) begin  
out_reg= B * D;  
end  
assign Out=out_reg;  
endmodule
```

```
module N_BIT_ADDER (D,B,SEL,C);  
parameter N=18;  
input [N-1:0] B;  
input [N-1:0] D;  
input SEL;  
output reg [N-1:0] C;  
always @(*) begin  
if (SEL)  
C = D-B;  
else  
C = D+B;  
end  
endmodule
```